

Current, Resistance and Potential Difference **Answers**

Potential difference can be calculated using the equation:

$$\text{potential difference} = \text{current} \times \text{resistance}$$

1. What is the potential difference if a current of 3A flows through a resistance of 20Ω?

$$\begin{aligned}\text{potential difference} &= 3 \times 20 \\ &= 60\end{aligned}$$

potential difference = **60V**

2. A current of 150mA passes through a 10Ω resistor.

Calculate the potential difference across the resistor.


$$\frac{150\text{mA}}{1000} = 0.15\text{A}$$

$$\begin{aligned}\text{potential difference} &= 0.15 \times 10 \\ &= 1.5\end{aligned}$$

potential difference = **1.5V**

3. **Figure 1** shows a series circuit.

Figure 1

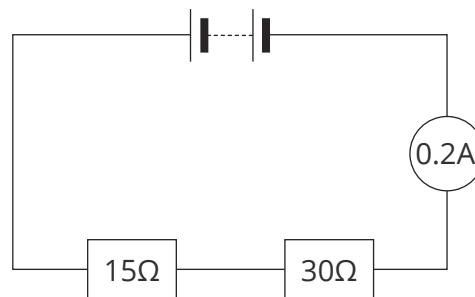

Calculate the potential difference across the battery.

$$15 + 30 = 45\Omega$$

$$\begin{aligned}\text{potential difference} &= 0.2 \times 45 \\ &= 9\end{aligned}$$

potential difference = **9V**

4. A 6V battery is connected across a filament lamp with a resistance of 40Ω .

Calculate the current through the lamp.

$$6 = \text{current} \times 40$$

$$\text{current} = \frac{6}{40}$$

$$= 0.15\text{A}$$

$$\text{current} = \mathbf{0.15\text{A}}$$

5. A 1.5V battery is connected across a 50Ω resistor.

Calculate the current through the resistor.

Give your answer in mA.

$$1.5 = \text{current} \times 50$$

$$\text{current} = \frac{1.5}{50}$$


$$= 0.03\text{A}$$

$$0.03 \times 1000 = 30\text{mA}$$

$$\text{current} = \mathbf{30\text{mA}}$$

6. **Figure 2** shows a parallel circuit.

Figure 2

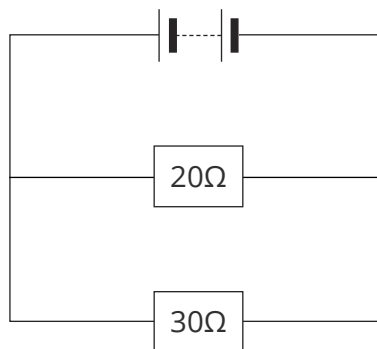

The potential difference across the battery is 6V.

Calculate the current through the 20Ω resistor.

$$6 = \text{current} \times 20$$

$$\text{current} = \frac{6}{20}$$

$$= 0.3\text{A}$$

$$\text{current} = \mathbf{0.3\text{A}}$$

7. A 12V battery causes a current of 3A to flow through a circuit.

Calculate the resistance of the circuit.

$$12 = 3 \times \text{resistance}$$

$$\begin{aligned} \text{resistance} &= \frac{12}{3} \\ &= 4\Omega \end{aligned}$$

resistance = **4Ω**

8. A potential difference of 6V causes a current of 200mA to flow through a circuit.

Calculate the resistance of the circuit.

$$\frac{200\text{mA}}{1000} = 0.2\text{A}$$


$$6 = 0.2 \times \text{resistance}$$

$$\begin{aligned} \text{resistance} &= \frac{6}{0.2} \\ &= 30\Omega \end{aligned}$$

resistance = **30Ω**

9. **Figure 3** shows a parallel circuit.

Figure 3

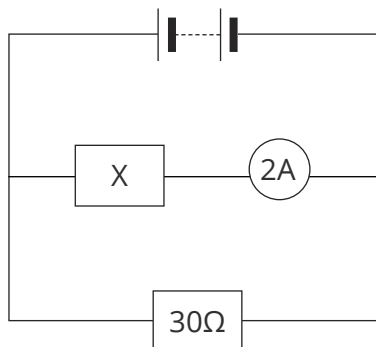

The potential difference across the battery is 9V.

Calculate the resistance of resistor **X**.


$$9 = 2 \times \text{resistance}$$

$$\begin{aligned} \text{resistance} &= \frac{9}{2} \\ &= 4.5\Omega \end{aligned}$$

resistance = **4.5Ω**

10. A student set up the circuit in **Figure 4**.

Figure 4

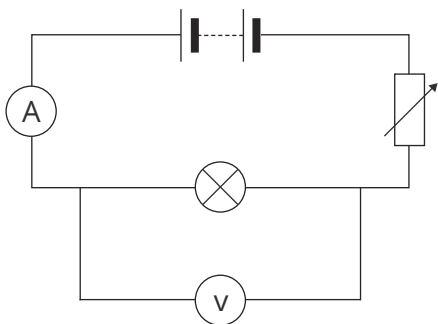

Describe how the student could use the circuit in **Figure 4** to investigate how the current through the lamp affects its resistance.

Mark Scheme	Mark
Level 3: There is a clear and logically ordered description of the method that could be followed to obtain valid results.	5-6
Level 2: There is a clear description of a method that may not produce valid results.	3-4
Level 1: There are simple statements that give a brief description of parts of the method. Two marks can be awarded for two correct statements.	1-2
No relevant content.	0
Indicative content: <ul style="list-style-type: none"> • An ammeter is used to measure current. • A voltmeter is used to measure potential difference. • The resistance of the variable resistor is altered to change the current in the circuit or change the potential difference across the lamp. • Five or more different values for current have been used (to allow for a valid conclusion). • $\text{resistance} = \frac{\text{potential difference}}{\text{current}}$ • Repeats of each value of current are taken. • A mean is calculated. 	