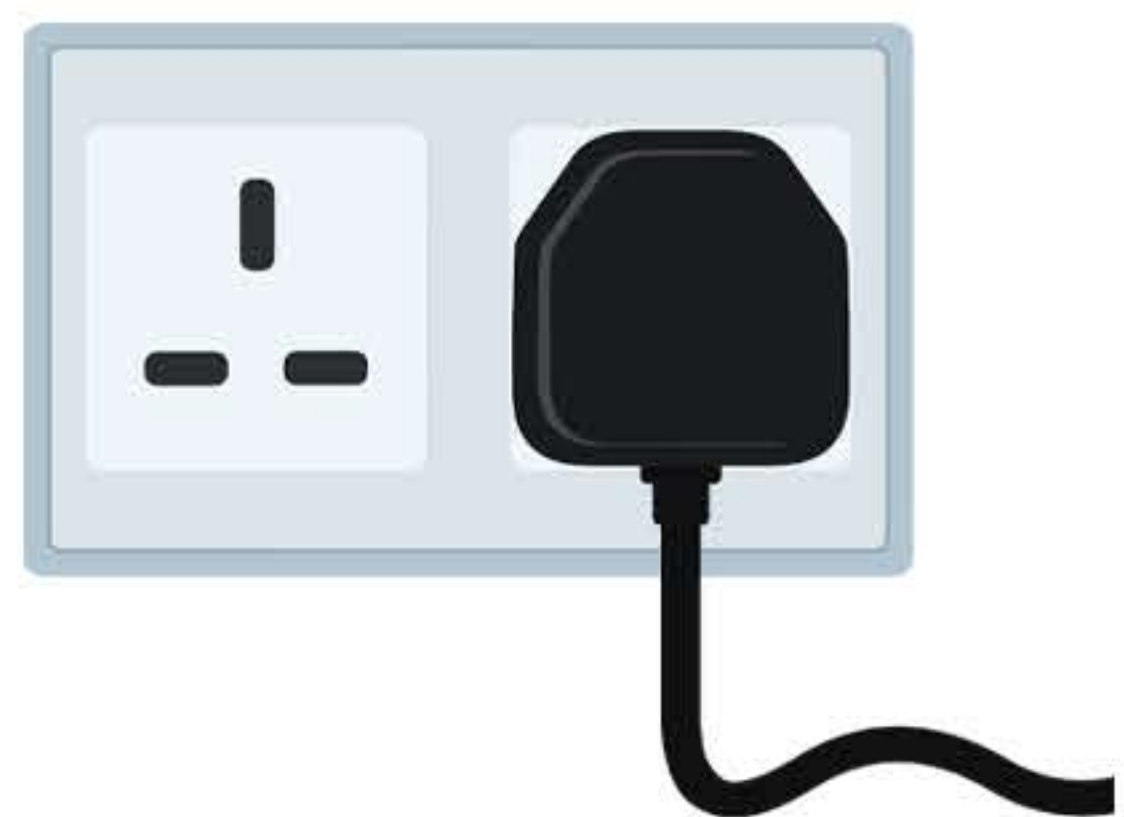





Electrical components




Cut out the components. Choose three to stick into the circuits below so that:


- All the circuits are silent
- Something is moving in at least one circuit
- You make the brightest bulb possible in one circuit

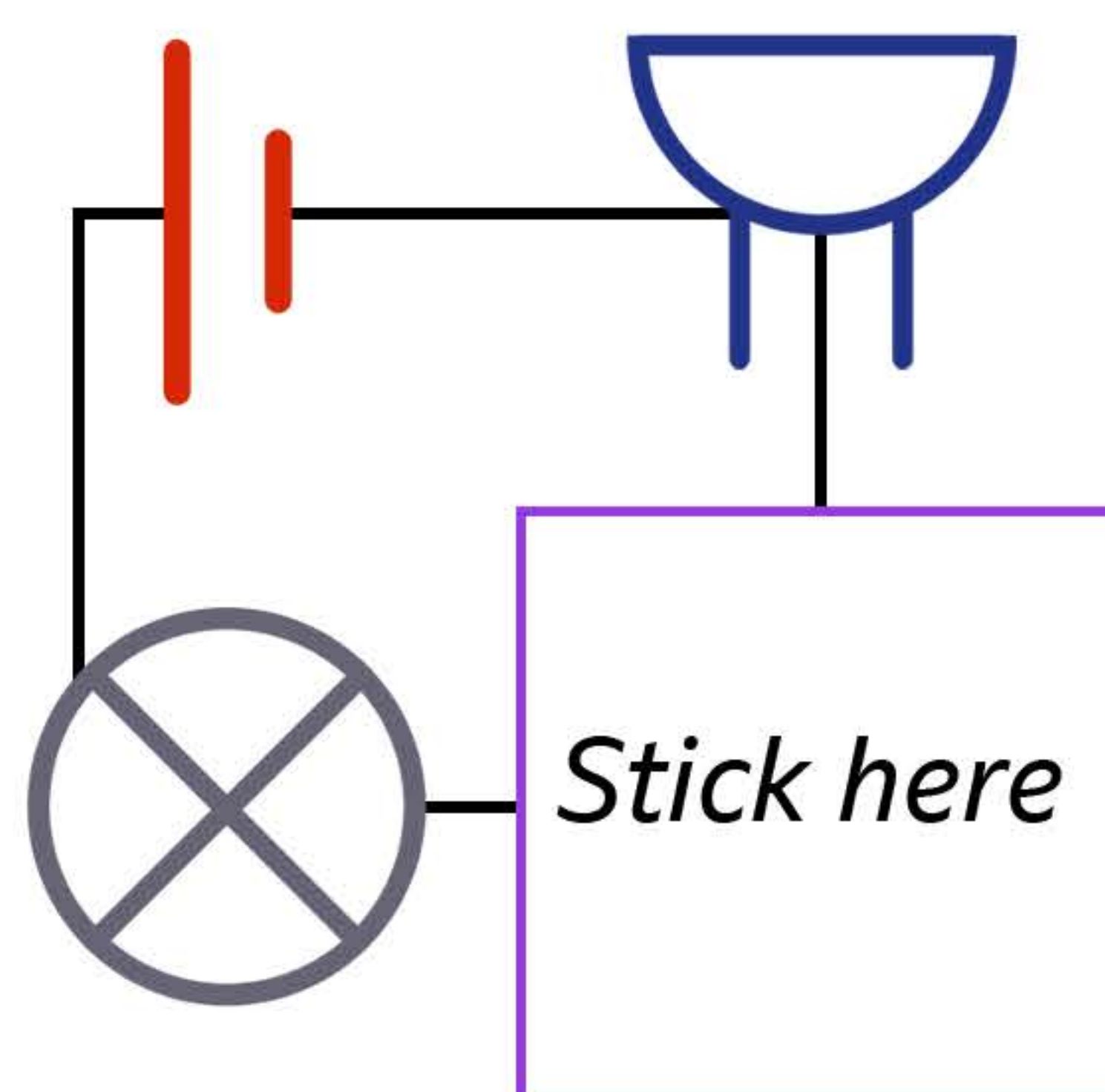

Circuit 1

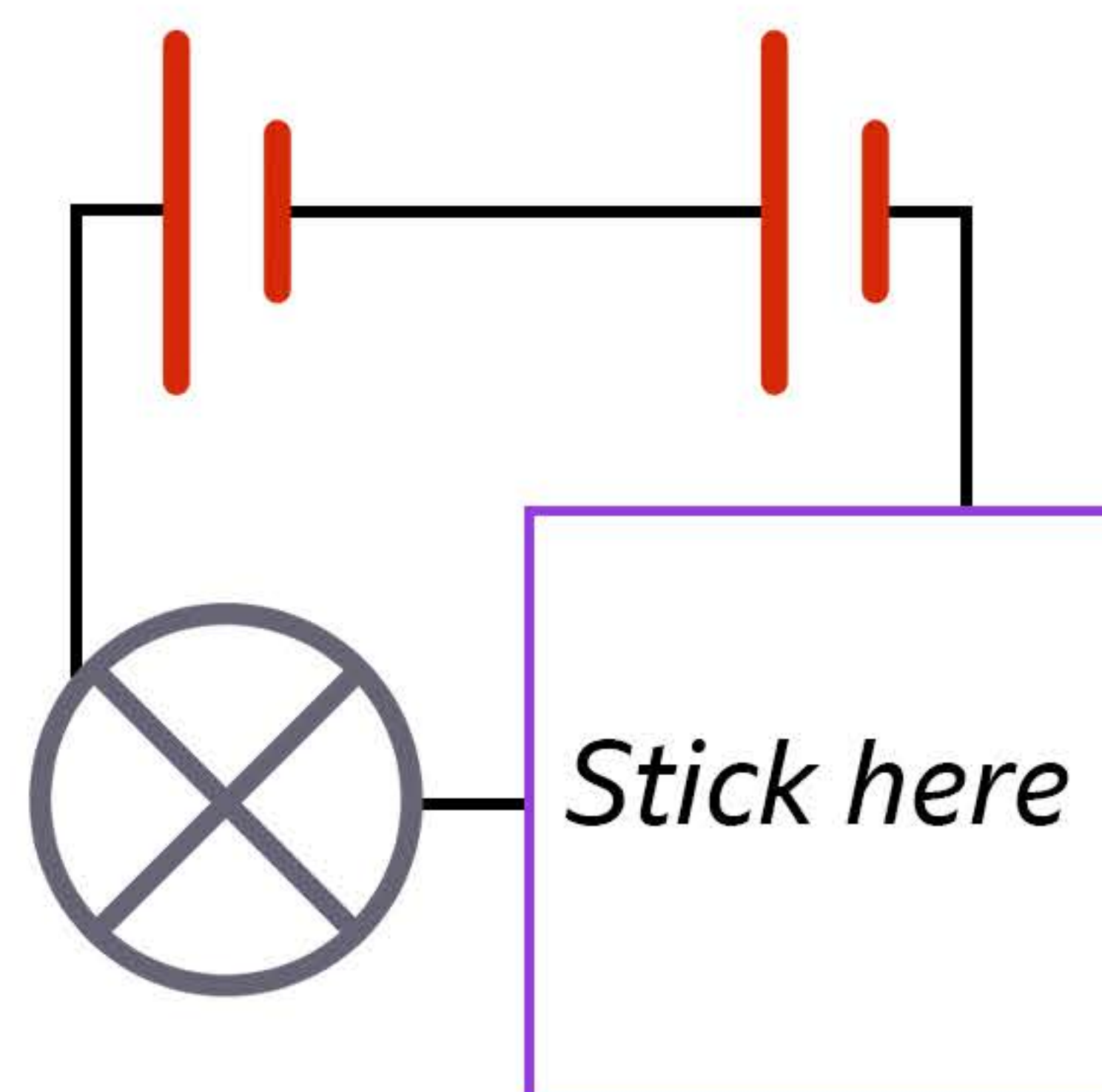

Circuit 3

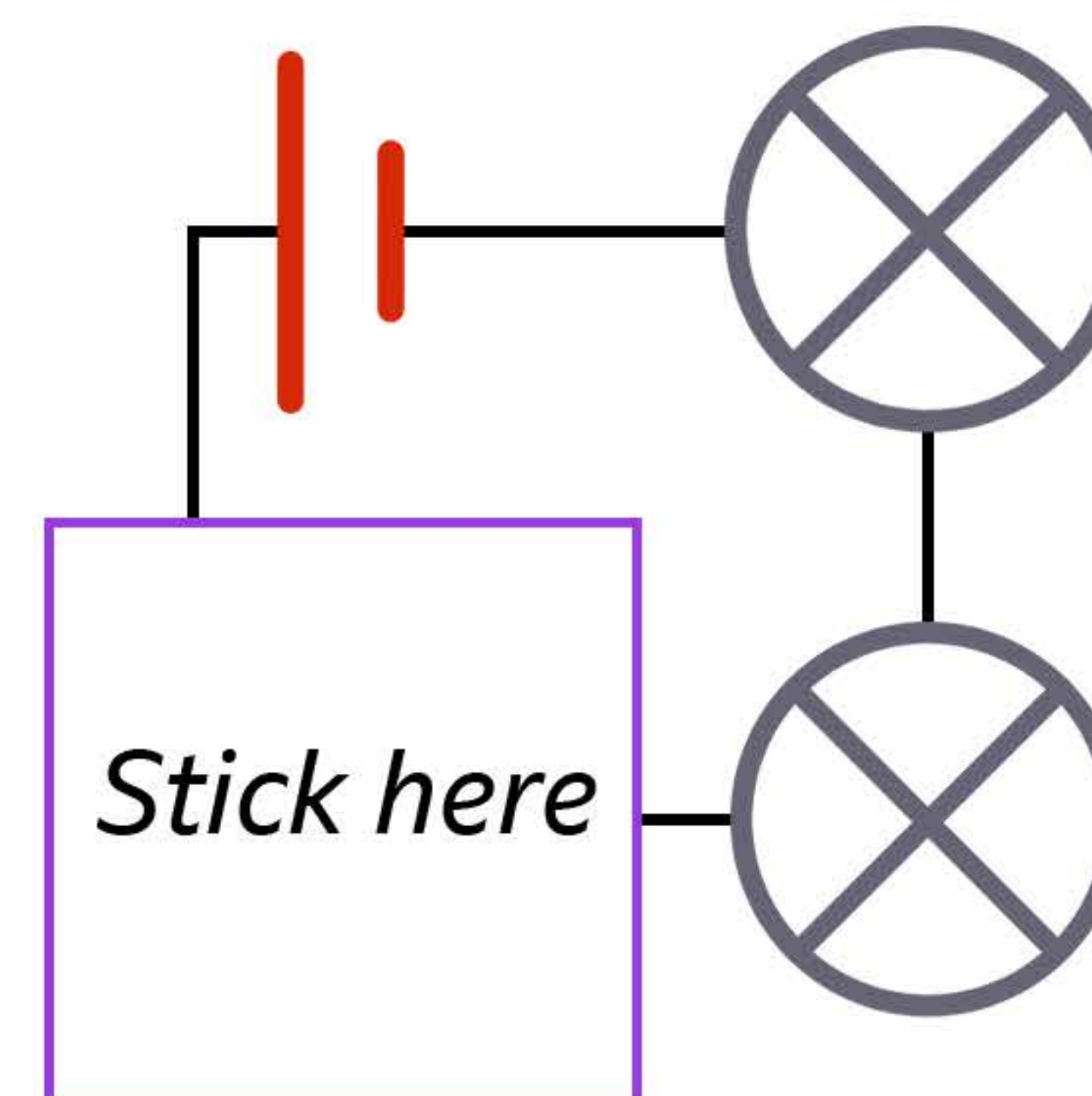

Circuit 2

