

# What are electrical circuits?

1. Create your own **circuit**.
2. **Remember:** It needs a **power source** (like a battery) to start with, from there you can add any of the **components** in the **box below**, they must all be connected by **wires** to work.
3. Can you make a **circuit** that uses all of the **components**?

